
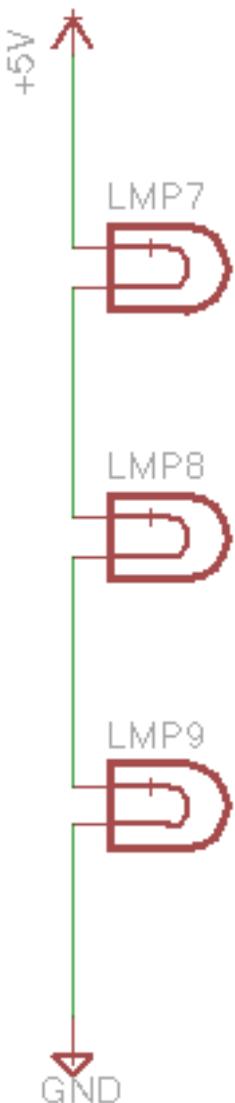


SERIES AND PARALLEL CIRCUITS


3.

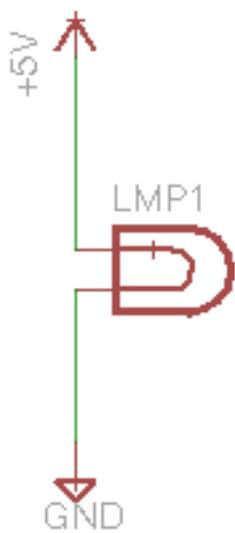


1.



2.

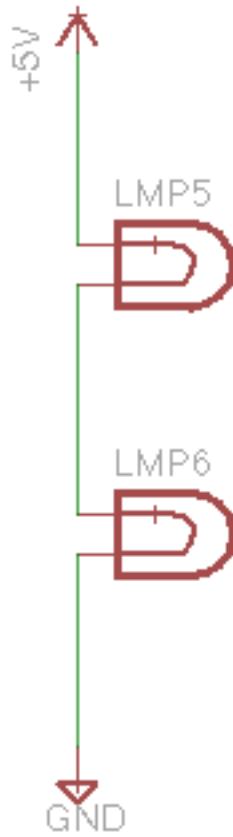

4.

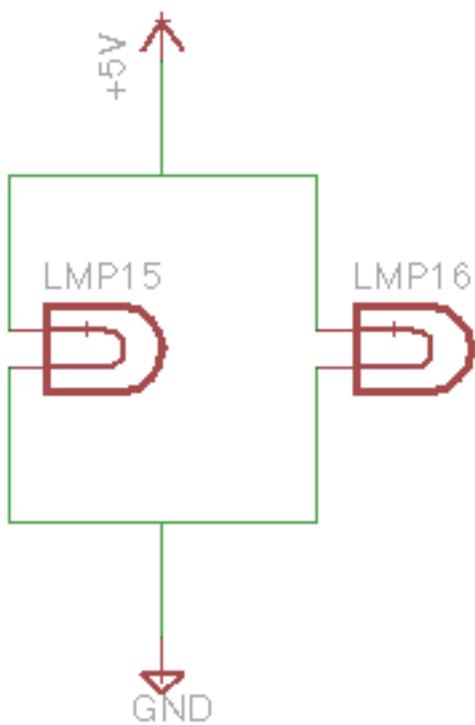

For each of these diagrams, label the relative brightness of each bulb. **Use a scale of 1 to 5, with 1 being brightest, and 5 being dimmest.** To get you started, the bulb in diagram #1 will have a brightness of "1". If you aren't sure with any of these, build it on your board and see how it behaves!

